# R UIR

#### **International Journal of Research**

Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

# Design and Implementation of Low Power Single Phase Clock Distributon

B.Vidya Sagar Goud & Mr. G.Sai Kumar

1.Pg Scholar, Department Of Ece, Ashoka Institute Of Engineering And Technology Malkapur(V), Choutuppal(M), Nalgonda(D)

2. Assistant Professor, Department Of Ece, Ashoka Institute Of Engineering And Technology Malkapur(V), Choutuppal(M), Nalgonda(D)

#### **ABSTRACT**

The clock distribution network consumes nearly 70% of the total power consumed by the IC since this is the only signal which has the highest switching activity. Normally for a multi clock domain network we develop a multiple PLL to cater the need, this project aim for developing a low power single clock multiband network which will supply for the multi clock domain network. This project is highly useful and recommended for communication applications like Bluetooth, Zigbee. WLAN frequency synthesizers are proposed based on pulse-swallow topology and the designed is modeled using Verilog simulated using Modelsim and implemented in Xilinx.

#### **I INTRODUCTION**

LAN (WLAN) in the multigigahertz bands such as HiperLAN II and IEEE 802.11a/b/g, are recognized as leading standards for high-rate data transmissions, and standards like IEEE802.15.4 are recognized for low-rate data

transmissions. The demand for lower cost, lower power, and multiband RF circuits increased in conjunction with need of higher level of integration. The frequency synthesizer, usually implemented by a phase-locked loop (PLL), is one of the power-hungry blocks in the RF frontend and the first stage frequency divider consumes a large portion of power in frequency synthesizer. The integrated synthesizers for WLAN applications at 5 GHz consume up to 25 mW in CMOS realizations, where the first-stage divider is implemented using an injection-locked divider which consumes large chip area and has a narrow locking range. The best published frequency synthesizer at 5 GHz consumes 9.7 mWat 1V supply, where its complete divider consumes power around 6 mW, where the firststage divider is implemented using the sourcecoupled logic (SCL) circuit which allows higher operating frequencies but uses more power. Dynamic latches are faster and consume less



Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

power compared to static dividers. The TSPC and E-TSPC designs are able to drive the dynamic latch with a single clock phase and avoid the skew problem. However, the adoption of single-phase clock latches in frequency dividers has been limited to PLLs with applications below 5 GHz .. Proposed dynamic logic multiband flexible Divider. The frequency synthesizer uses an E-TSPC prescaler as the first-stage divider, but the divider consumes around 6.25 mW. Most IEEE 802.11a/b/g frequency synthesizers employ SCL dividers as their first stage while dynamic latches are not yet adopted for multiband synthesizers. In this paper, a Dynamic logic multiband flexible integer-n divider based on pulse-swallow topology is proposed which uses a low-power wideband 2/3 prescaler and a wideband multimodulus 32/33/47/48 prescaler as shown in Fig.1 The divider also uses an improved low power loadable bit-cell for the Swallow Scounter. II.DESIGN CONSIDERATIONS

The key parameters of high-speed digital circuits are the propagation delay and power consumption. The maximum operating frequency of a digital circuit is calculated and is given by

f max = 1/tpLH+tpHL (1)

Where tpLH and tpHL are the propagation delays of gates, respectively. The total power consumption of the CMOS digital circuits is determined by the switching and short circuit power. The switching power is linearly Wproportional to the operating frequency and is given by the sum of switching power at each output node as in P

switching =  $\sum$  fclkCLiV 2 dd (2)

Where n is the number of switching nodes, fclk is the clock frequency, CLi the load capacitance at the output node of the ith stage, and vdd is the supply voltage. Normally the shortcircuit power occurs in dynamic circuits when there exists direct paths from the supply to ground which is given by

PSC=ISC\*vdd (3)

Where ISC is the short-circuit current. The analysis in ETSPC shows that the short-circuit power is much higher in E-TSPC logic circuits than in TSPC logic circuits. However, TSPC logic circuits exhibit higher switching power compared to that of E-TSPC logic circuits due to high load capacitance. For the E-TSPC logic circuit, the short-circuit power is the major problem. The E-TSPC circuit has the merit of higher operating frequency than that of the TSPC circuit due to the reduction in load



Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

capacitance, but it consumes significantly more power than the TSPC circuit does for a given transistor size. The following analysis is based on the latest design using the popular and low-cost 0.18µ CMOS process.

A.Swallow (S) Counter The 6-bit s-counter shown in Fig.4.consists of six asynchronous loadable bit-cells, a NOR-embedded DFF and additional logic gates to allow it to be programmable from 0 to 31 for low-frequency band and from 0 to 47 for the highfrequency band. The asynchronous bit cell used in this design shown in Fig.4.is similar to the bit-cell except it uses two additional transistors M6 and M7whose inputs are controlled by the logic signal MOD. If MOD is logically high, nodes S1 and S2 switch to logic "0" and the bit-cell does not perform any function. The MOD signal goes logically high only when the S-counter finishes counting down to zero. If MOD and LD are logically low, the bit-cell acts as a divide-by-2 unit. If MOD is logically low and LD is logically high, the input bit PI is transferred to the output. In the initial state, MOD=0, the multimodulus prescaler selects the divide-by-N+1 mode (divide-by-33 or divide-by-48) and P, S counters start down counting the input clock cycles. When the S-counter finishes counting, MOD switches to logic "1" and the prescaler changes to the divide-by-n mode (divide-by-32

or divide-47) for the remaining P-S clock cycles. During this mode, since Scounter is idle, transistors M6 and M7 which are controlled by MOD, keep the nodes S1 and S2 at logic "0," thus saving the switching power in S-counter for a period of (N\*(P-S)) clock cycles. Here, the programmable input (PI) is used to load the counter to a specified value from 0 to 31 for the lower band and 0 to 48 for the higher band of operation.

# III. Programmable (P) Counter

The programmable P-counter is a 7-bit asynchronous down counter which consists of 7 loadable bit-cells and additional logic gates. Here, bit P7 is tied to the Sel signal of the multi modulus prescaler and bits P4 and P7 are always at logic "1." The remaining bits can be externally programmed from 75 to 78 for the lower frequency band and from 105 to 122 for the upper frequency band. When the P-counter finishes counting down to zero, LD switches to logic "1" during which the output of all the bitcells in S-counter switches to logic "1" and output of the NOR embedded DFF switches to logic "0" (MOD=0) where the programmable divider get reset to its initial state and thus a fixed division ratio is achieved. If a fixed 32/33 (N/(N+1)) dual-modulus prescaler is used, a 7bit P-counter is needed for the lowfrequency band

# R

## **International Journal of Research**

Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

(2.4 GHz) while an 8-bit S-counter would be needed for the high frequency band(5–5.825 GHz) with a fixed 5-bit S-counter. Thus, the multimodulus32/33/47/48 prescaler eases the design complexity of the P-counter.

1)When Sel="0": When Sel="0" the output from N4 gate is given to the prescaler and the multimodulus prescaler selects 32/33 mode and the division ratio is controlled by MOD signal. When MOD=1 the output from N4 gate switches to logic ",1" and the prescaler operates in divideby-2 for entire operation. i.e., now division ratio of 32 (N) is performed. Similarly when MOD=0, MC remains high for first 30 input clock cycles and goes low for 3 input clock cycles. Thus division ratio of 33(N+1) is performed. N and N+1 are given by 32 = (AD\*N1) = N (33=1) + N = N (33=1)(1\*(N1+1)\*N1) - ((AD = 1+N 2)When Sel=1:When Sel=1, the inverted output from N4 gate is given to the input of 2/3 prescaler and multimodulus prescaler operates in 47/48 mode. MOD signal controls the division ratio. When MOD=1 and MC=1 prescaler operated in divideby-3 for the entire input cycles and division ratio of 48(N+1) is performed. When MOD=1 and MC=0 divideby- 2 is selected for entire input clock cycles for prescaler and the division ratio of 47(N) is performed. N and N+1 are given by

# IV.SIMULATION RESULTS

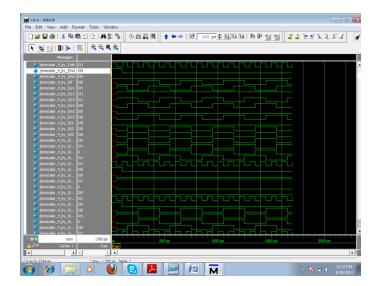


Fig. 4.1 Simulation Result

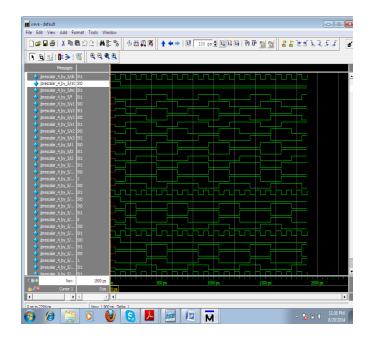


Fig. 4.2 Simulation Result



Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

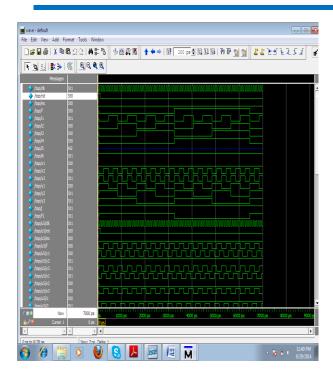


Fig. 4.3 Simulation Result

## A. SYNTHESIS RESULTS

#### **B.HDL SYNTHESIS REPORT**

**Macro Statistics** 

# Registers : 7

1-bit register : 7

#### C.FINAL REGISTER REPORT

**Macro Statistics** 

# Registers : 6

Flip-Flops : 6

#### **D.DEVICE UTILIZATION SUMMARY:**

Device utilization summary:

Selected Device: 3s500efg320-5

Number of Slices: 3 out of 4656

0%

Number of Slice Flip Flops: 6 out of

9312 0%

Number of 4 input LUTs: 5 out of

9312 0%

Number of IOs: 4

Number of bonded IOBs: 3 out of

232 1%

Number of GCLKs: 1 out of

24 4%

#### E. TIMING SUMMARY

Speed Grade: -5

Minimum period: 2.131ns (Maximum

Frequency: 469.274MHz)

Minimum input arrival time before clock:

2.470ns

Maximum output required time after clock:

4.063ns

#### F. RTL SCHEMATIC

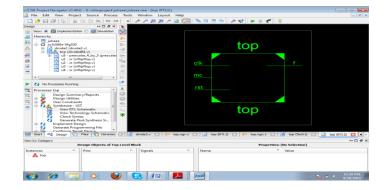


Fig. 4.4 Top Level Circuit



Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

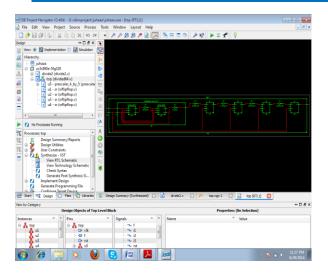


Fig4.5 Rtl Schematic diagram

#### G.TECHNOLOGY SCHEMATIC

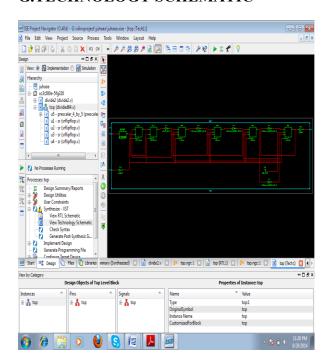


Fig. 4.6 Technology Schematic

#### IV CONCLUSION

In this paper, a wideband 2/3 prescaler is verified in the design of proposed wide band multi modulus 32/33/47/48 prescaler. A dynamic

logic multiband flex-ible integer N divider is designed which uses the wide-band prescaler, multi modulus 32/33/47/48 prescaler, and is silicon verified using the 0.18µm CMOS technology. Since the multi modulus 32/33/47/48 prescaler has maximum operating frequency of 6.2 GHz, the values of P- and Scounters can actually be programmed to divide over the whole range of frequencies from 1 to 6.2 GHz with finest resolution of 1 MHz and variable chan-nel spacing. However, since interest lies in the 2.4- and 5-5.825-GHz bands the P- and S-counters are of operation, programmed accordingly. The proposed multiband flexible divider also uses an improved loadable bit-cell for Swallow S-counter and consumes a power of 0.96 and 2.2 mW in 2.4and 5-GHz bands, respectively, and provides a solution to the low power PLL synthesizers for Bluetooth, Zigbee, IEEE 802.15.4, and IEEE 802.11a/ b/g WLAN applications with variable channel spacing.

#### **REFERENCES:**

1.H. R. Rateghet al., "A CMOS frequency synthesizer with an injectedlocked frequency divider for 5-GHz wir-less LAN receiver," IEEE J. Solid-State Circuits, vol. 35, no. 5, pp. 780–787, May 2000.

2.P. Y. Deng et al., "A 5 GHz frequency synthesizer with an injectionlockedfrequency



Available at https://edupediapublications.org/journals

e-ISSN: 2348-6848 p-ISSN: 2348-795X Volume 05 Issue-01 January 2018

divider and differential switched capacitors," IEEE Trans. Circuits Syst. I, Reg. Papers, vol. 56, no. 2, pp. 320–326, Feb. 2009.

- 3.L. Lai Kan Leung et al., "A 1-V 9.7-mW CMOS fre-quency synthesizer for IEEE 802.11a transceivers," IEEE Trans. Microw. Theory Tech., vol. 56, no. 1, pp. 39–48, Jan. 2008.
- 4.M. Alioto and G. Palumbo, Model and Design of Bipo-lar and MOS Current-Mode Logic Digital Circuits. New York: Springer, 2005.
- 5.Y. Ji-renet al., "Atrue single-phase-clock dynamicC-MOScircuit technique," IEEE J. Solid-State Circuits, vol. 24, no. 2, pp. 62–70, Feb.1989.
- 6.S. Pelleranoet al., "A 13.5-mW 5 GHz frequency synthesizer with dynamic-logic frequency divider," IEEE J. Solid-State Circuits, vol. 39, no. 2, pp. 378–383, Feb. 2004.
- 7.V. K. Manthenaet al., "A low power fully programmable 1 MHz resolution 2.4 GHz CMOS PLL frequency synthesizer," in Proc. IEEE Biomed. Circuits Syst. Conf., Nov. 2007, pp. 187–190.

- 8.S. Shin et al., "4.2 mW frequency synthesizer for 2.4 GHz ZigBee application with fast settling time performance," in IEEE MTT-S Int. Microw. Symp. Dig., Jun. 2006, pp. 411–414.
- 9.S. Vikaset al., "1 V 7-mW dual-band fast-locked frequency synthesizer," in Proc. 15th ACM Symp. VLSI, 2005, pp. 431–435.
- 10. V. K. Manthenaet al., "A 1.8-V 6.5-GHz low power wide band singlephase clock CMOS 2/3 prescaler," in IEEE 53rd Midwest Symp. Circuits Syst., Aug. 2010, pp. 149–152.
- 11.J. M. Rabaeyet al., "Digital integrated circuits, a design perspective," in Ser. Electron and VLSI, 2nd ed. Upper Saddle River, NJ: Prentice- Hall, 2003.
- 12.X. P. Yu et al., "Design and optimization of the extended true singlephase clock-based prescaler," IEEE Trans. Microw. Theory Tech., vol. 56, no. 11, pp. 3828–3835, Nov. 2006.
- 13.X. P. Yu et al., "Design of a low power wideband high resolution programmable frequency divider," IEEE Trans. Very Large Scale Integr. (VLSI) Syst., vol. 13, no. 9, pp. 1098–1103, Sep. 2005